

**BRAC UNIVERSITY**  
**DEPT. OF COMPUTER SCIENCE AND ENGINEERING**  
**COURSE NO.: CSE250**  
**Circuits and Electronics Laboratory**

**Experiment No. 2**

**Name of the Experiment:**

**Verification of KCL and KVL**

**KVL**

**OBJECTIVE:**

This experiment is intended to verify Kirchhoff's voltage law (KVL) with the help of series circuits.

**THEORY:**


KVL states that around any closed circuit the algebraic sum of the voltage rises equals the algebraic sum of the voltage drops.

**APPARATUS:**

- One DC Ammeter (0 - 1A)
- One multimeter
- Three Resistors
- One DC power supply

**PROCEDURE:**

- Connect the resistors  $R_1$ ,  $R_2$  and  $R_3$  in series to a DC power supply as shown in Fig 1.

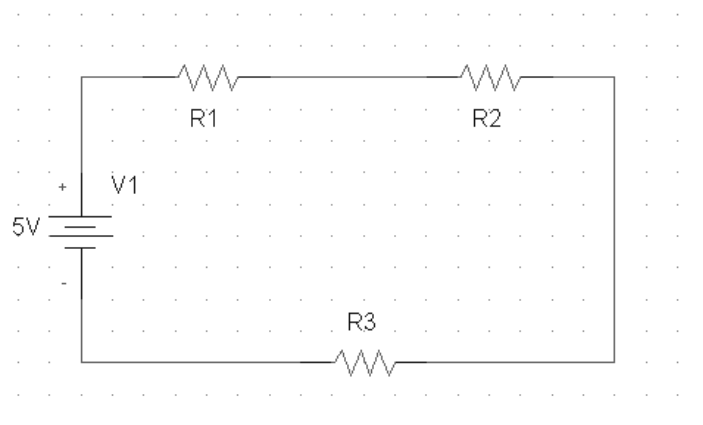

**Fig. 1**

- Take readings of  $V_1$ ,  $V_2$ ,  $V_3$ ,  $V_s$  using multimeter . Take two sets of reading and enter them in the table shown below

- Verify KVL as  $V_S = V_1 + V_2 + V_3$  for each set of readings.
- Calculate the theoretical values of  $V_1$ ,  $V_2$  &  $V_3$  & note them down in 'Theoretical Observation' row in table  
Use voltage divider rule as stated below to get these values:

$$V_1 = (R_1 / R_e) * V;$$

$$V_2 = (R_2 / R_e) * V;$$

$$V_3 = (R_3 / R_e) * V$$

$$\text{Where, } R_e = R_1 + R_2 + R_3$$

**TABLE 1:** Verification of KVL.

Observation	R1	R2	R3	V	V1	V2	V3
Experimental							
Theoretical							

### REPORT:

1. State the rules of connecting voltmeter and ammeter in the circuit.
2. Comment on the results obtained and discrepancies (if any).

## KCL

### OBJECTIVE:

This experiment is intended to verify Kirchhoff's current law (KCL) with the help of a simple parallel circuit.

### THEORY:

KCL states that the algebraic sum of the currents entering any node equals the sum of the currents leaving the node.

### APPARATUS:

- One DC Ammeter (0 - 1A)
- Three resistors
- One multimeter
- One DC supply

## PROCEDURE:

- Connect the resistors in parallel across the power supply as shown in figure2

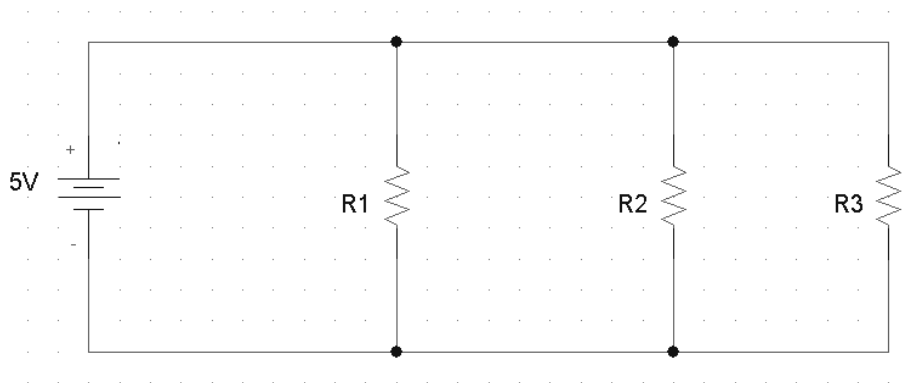


Fig.2

- Measure  $V_s$ ,  $I_o$ ,  $I_1$ ,  $I_2$ ,  $I_3$ . Take two sets of reading.
  - Verify KCL as  $I_s = I_1 + I_2 + I_3$  for each set of readings.
  - Calculate the theoretical values of  $I$ ,  $I_1$ ,  $I_2$  &  $I_3$  & note them down in 'theoretical observation' row in table
- Use the following to get these values:

$$I_1 = V/R_1; \quad I_2 = V/R_2; \quad I_3 = V/R_3; \quad I = I_1 + I_2 + I_3$$

**TABLE 1:** Verification of KCL.

Observation	R1	R2	R3	V	I	I1	I2	I3
Experimental								
Theoretical								

## REPORT:

1. Comment on the obtained results and discrepancies (if any).